

**Learning Objective: Small Signal Parameters****Problem 1.** Consider the following  $I_D$  equation

$$I_D = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

Show the following equality.

$$(a) \quad g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = 2K_n (V_{GS} - V_{TH})$$

$$\begin{aligned} g_m &= \frac{\partial I_D}{\partial V_{GS}} \\ &= \frac{\partial}{\partial V_{GS}} \left[ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \right] \\ &= (2) \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) (1) \\ &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \\ &= 2K_n (V_{GS} - V_{TH}) \end{aligned}$$

$$(b) \quad g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = 2\sqrt{K_n I_D}$$


$$\begin{aligned} g_m^2 &= \left[ \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \right]^2 \\ &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \left[ \mu_n C_{ox} \frac{W}{L} \right] \\ &= (2) \left[ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \right] \left[ \mu_n C_{ox} \frac{W}{L} \right] \\ &= 2I_D \left[ \mu_n C_{ox} \frac{W}{L} \right] \\ &= 2\mu_n C_{ox} \frac{W}{L} I_D \\ g_m &= \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = 2\sqrt{K_n I_D} \end{aligned}$$

$$(c) \quad g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$\begin{aligned} g_m &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \\ &= \frac{1}{2} (2) \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \times \frac{V_{GS} - V_{TH}}{V_{GS} - V_{TH}} \\ &= \frac{(2) \left[ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \right]}{V_{GS} - V_{TH}} \\ &= \frac{2I_D}{V_{GS} - V_{TH}} \end{aligned}$$

**Learning Objective: Maximum Voltage Swing Configuration**

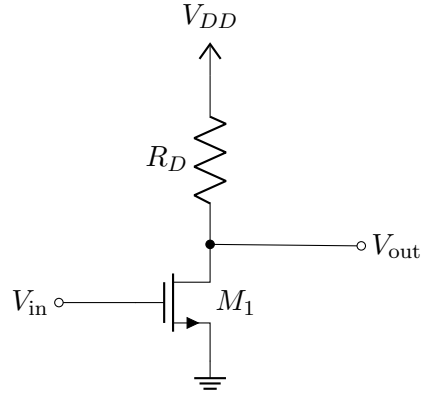**Problem 2.** Consider a resistive load common source amplifier below, where  $R_D = 1 \text{ k}\Omega$  and  $V_{DD} = 5 \text{ V}$ . The n-channel MOSFET has a threshold voltage  $V_{TH} = 0.7 \text{ V}$ , conduction parameter  $K_n = 0.5 \text{ mA/V}^2$ . Assume  $\lambda = 0$ ,  $\gamma = 0$ .



- (a) Determine the **range of output voltage  $V_{out}$**  to operate the MOSFET  $M_1$  in saturation region.

The maximum  $V_{out}$  occurs when the MOSFET is biased at  $V_{in}$  slightly larger than the threshold voltage, makes a current  $I_{DS}$  close to 0 A, so  $V_{out}^{\max} = V_{DD} = 5 \text{ V}$ . The minimum  $V_{out}$  to keep the MOSFET in saturation is when MOSFET is biased at the edge of the saturation region ( $V_{DS} = V_{GS} - V_{TH}$ ), therefore:

$$\begin{aligned}
 V_{DD} - I_D R_D &= V_{DS} \\
 V_{DD} - K_n (V_{GS} - V_{TH})^2 R_D &= V_{DS} \\
 V_{DD} - K_n (V_{DS})^2 R_D &= V_{DS} \\
 (5) - (0.5)(V_{DS})^2 (10) &= V_{DS} \\
 V_{DS} &= V_{out}^{\min} = 2.317 \text{ V}
 \end{aligned}$$

- (b) Determine the **range of input voltage  $V_{in}$**  to operate the MOSFET  $M_1$  in saturation region.

The minimum  $V_{in}$  occurs when it's slightly larger than the threshold voltage, so  $V_{in}^{\min} = V_{TH} = 0.7 \text{ V}$ . The maximum  $V_{in}$  that keep the MOSFET in saturation occurs when the MOSFET is biased edge of the saturation region ( $V_{DS} = V_{GS} - V_{TH}$ ), with  $V_{out}^{\min}$  calculated above:

$$\begin{aligned}
 V_{DD} - I_D R_D &= V_{out}^{\min} \\
 I_D^{\max} &= \frac{V_{DD} - V_{out}^{\min}}{R_D} \\
 &= \frac{(5) - (2.317)}{1000} = 2.68 \text{ mA} \\
 K_n (V_{in}^{\max} - V_{TH})^2 &= 2.68 \times 10^{-3} \\
 (0.5 \times 10^{-3})(V_{in}^{\max} - 0.7)^2 &= 2.68 \times 10^{-3} \\
 V_{in}^{\max} &= 3.015 \text{ V}
 \end{aligned}$$

- (c) Assume the MOSFET operates at the center of the saturation region, determine the **Q-point of the MOSFET** ( $V_{DS}$ ,  $I_D$ ) and the **input voltage**  $V_{in}$ .

$$V_{DS}^Q = \frac{V_{out}^{\max} + V_{out}^{\min}}{2} = 3.659 \text{ V}$$

$$I_D^Q = I_D^{\max}/2 = 1.34 \text{ mA}$$


$$= K_n(V_{GS}^Q - V_{TH})^2$$

$$= (0.5)(V_{GS}^Q - 0.7)^2$$

$$V_{GS}^Q = 2.337 \text{ V}$$

**Learning Objective:** Common Source Amplifier without  $R_s$

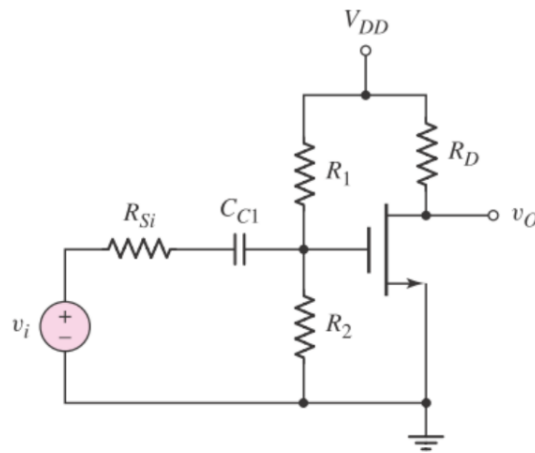**Problem 3.** A common-source amplifier circuit has following parameters:  $K_n = 0.6 \text{ mA/V}^2$ ,  $V_{DD} = 3.5 \text{ V}$ ,  $R_D = 12 \text{ k}\Omega$ ,  $R_1 = 144 \text{ k}\Omega$ ,  $R_2 = 65 \text{ k}\Omega$ ,  $R_{Si} = 12 \text{ k}\Omega$ ,  $V_{TN} = 0.5 \text{ V}$ , and  $\lambda = 0.018 \text{ V}^{-1}$ .



- (a) Determine  $I_{DQ}$ .

$$V_{GSQ} = V_G - V_S$$

$$= (V_{DD}) \frac{R_2}{R_1 + R_2} - 0$$

$$= (3.5) \frac{65}{144 + 65} = 1.088 \text{ V}$$

$$I_{DQ} = K_n(V_{GSQ} - V_{TH})^2$$

$$= (0.6)(1.088 - 0.5)^2$$

$$= 0.207 \text{ mA}$$

- (b) Prove that the transistor is biased in the saturation region.

$$V_{DSQ} = V_{DD} - I_{DQ}R_D$$

$$= 3.5 - (0.207)(12) = 1.016 \text{ V} > V_{GSQ} - V_{TH} = 1.088 - 0.5 = 0.588 \text{ V}$$

Therefore, the MOSFET is biased in the saturation.


- (c) Determine  $g_m$  and  $r_o$  for the small-signal FET model.

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2 \times 0.207 \times 10^{-3}}{0.588} = 0.704 \text{ mA/V}$$

$$r_o = [\lambda I_{DQ}]^{-1} = [(0.018)(0.207 \times 10^{-3})]^{-1} = 268.38 \text{ k}\Omega$$

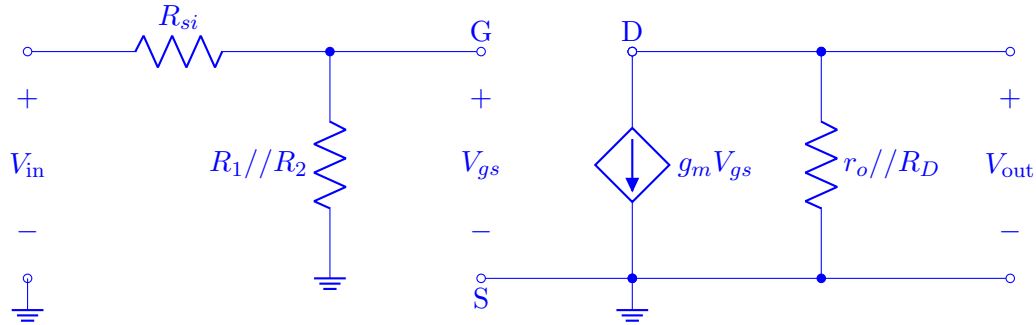- (d) Determine the **input and output resistances** of the common source amplifier.

The given circuit is converted to the following small signal model:



To calculate input resistance  $R_{in}$ , make  $V_{out} = 0 \text{ V}$ , then calculate the Thevenin equivalent resistance looking into  $V_{in}$  find

$$R_{in} = R_1 // R_2 = 44.784 \text{ k}\Omega$$

To calculate output resistance  $R_{out}$ , make  $V_{in} = 0 \text{ V}$ . The dependent current source is open because  $V_{in} = V_{gs} = 0 \text{ V}$  so that  $g_m V_{gs} = 0 \text{ A}$ . The Thevenin equivalent resistance looking into  $V_{out}$  find

$$R_{out} = R_D // r_o = 11.486 \text{ k}\Omega$$

- (e) Determine the small **signal voltage gain**.

From the small signal model in part (d), do KVL at  $V_{in}$  that gives:

$$V_{in} \times \frac{R_1 // R_2}{R_1 // R_2 + R_{si}} = V_{gs}$$

$$V_{gs} \left( \frac{R_1 // R_2}{R_1 // R_2 + R_{si}} \right)^{-1} = V_{in}$$

Do KCL at  $V_{out}$  that gives:

$$V_{out} = -g_m V_{gs} r_o // R_D$$

Therefore, the small signal gain can be expressed as:


$$A_v = V_{out} / V_{in}$$

$$= -g_m (r_o // R_D) \left( \frac{R_1 // R_2}{R_1 // R_2 + R_{si}} \right)$$

$$= -6.577$$


**Learning Objective: Common Source Amplifier with  $R_S$** 

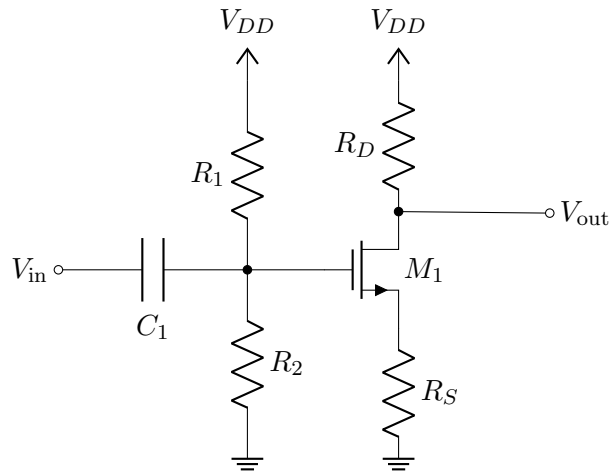**Problem 4.** Consider a resistive load common source amplifier below. Assume the MOSFET operates in saturation,  $R_S \neq 0$ ,  $\lambda = 0$ ,  $\gamma = 0$ .



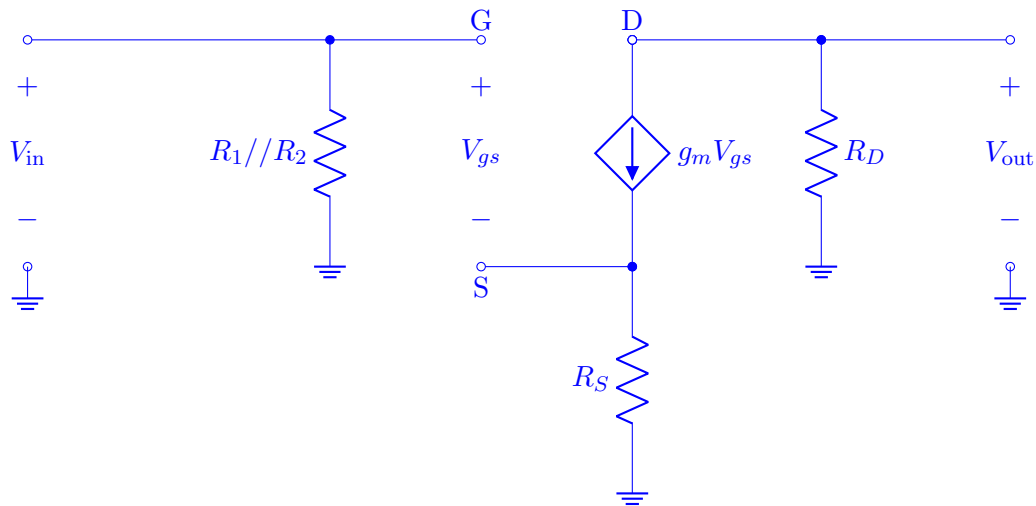- (a) Plot the **small signal equivalent circuit** of the given amplifier.

The given circuit is converted to the following small signal model:



- (b) Determine the **input and output resistances** of the common source amplifier.

To calculate input resistance  $R_{in}$ , make  $V_{out} = 0$  V, then calculate the Thevenin equivalent resistance looking into  $V_{in}$  find

$$R_{in} = R_1 // R_2$$

To calculate output resistance  $R_{out}$ , make  $V_{in} = 0$  V. Do KVL at  $V_{in}$  gives:

$$V_{gs} + g_m V_{gs} R_S = V_{in} = 0$$

$$V_{gs} (1 + g_m R_S) = 0$$

So that  $V_{gs} = 0$  V, due to  $(1 + g_m R_S)$  can't be zero. So that the output resistance is:

$$R_{out} = R_D$$

- (c) Derive an expression of the **output voltage** and **small-signal voltage gain**.

From the small signal model in part (a), do KCL at  $V_{out}$  that gives:


$$V_{out} = -g_m V_{gs} R_D$$

Therefore, the small signal gain can be expressed as:

$$A_v = V_{out}/V_{in} = \frac{-g_m R_D}{1 + g_m R_S}$$


### Learning Objective: Common Source Amplifier

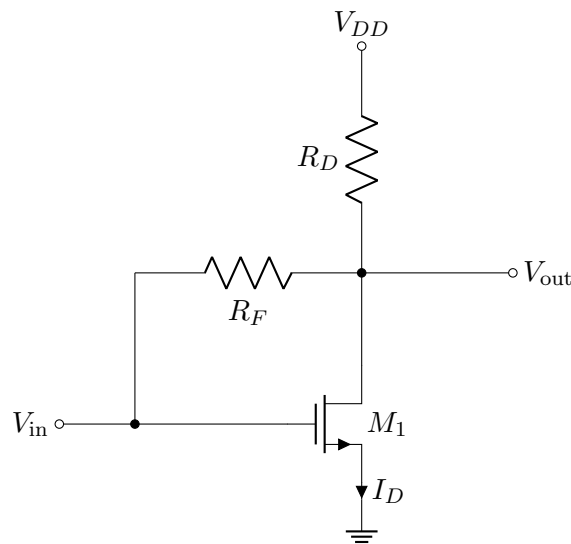**Problem 5.** Consider a resistive load common source amplifier below. Assume the MOSFET operates in saturation,  $\lambda \neq 0$ ,  $\gamma = 0$ .



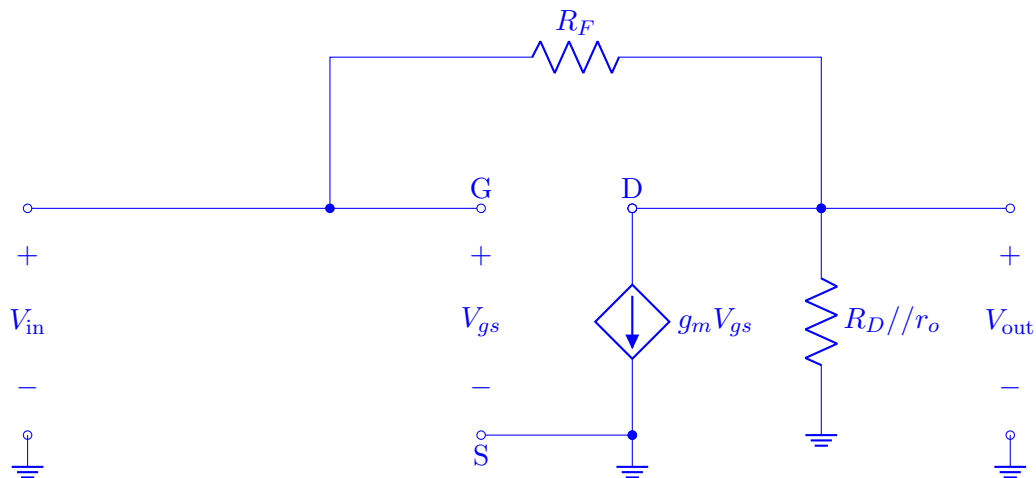- (a) Plot the **small signal equivalent circuit** of the given amplifier.

The given circuit is converted to the following small signal model:



- (b) Determine the expression of **output voltage** and **small-signal voltage gain**.

From the small signal model in part (a), do KCL at  $V_{\text{out}}$  gives:

$$\begin{aligned}\frac{V_{\text{out}}}{R_D//r_o} + g_m V_{gs} + \frac{V_{\text{out}}}{R_F} - \frac{V_{gs}}{R_F} &= 0 \\ V_{\text{out}} \left( \frac{1}{R_D//r_o} + \frac{1}{R_F} \right) &= V_{gs} \left( \frac{1}{R_F} - g_m \right) \\ V_{\text{out}} &= V_{gs} \left( \frac{1}{R_F} - g_m \right) \left( \frac{1}{R_D//r_o} + \frac{1}{R_F} \right)^{-1} \\ &= V_{gs} \left( \frac{1}{R_F} - g_m \right) (R_D//r_o//R_F) \\ A_v &= \left( \frac{1}{R_F} - g_m \right) (R_D//r_o//R_F)\end{aligned}$$